



॥ सा विद्या या विमुक्तये ॥

भारतीय प्रौद्योगिकी संस्थान धारवाड़

Indian Institute of Technology Dharwad

High Voltage Isolated Differential Probe

EE314: EDL Project

Team Members:

Shashi prabha	200020043
Mouli Venkata Prakash	200020027
Devi Prasad	200020022

Project Supervisor

Prof. Dr.Abhijit Kshirsagar
Dept. of Electrical Engineering IIT Dharwad

Project Timeline

A. First Evaluation

1. Study of existing solutions
2. Requirement Building / Spec freeze
3. High-level system Design by 27/Jan 2023

B. Second Evaluation

4. Simulation
5. Prototyping
6. PCB design by 17/Feb 2023

C. Third Evaluation

7. Prototyping and Assembling
8. Integration 17/March 2023

D. Final Evaluation

9. Testing and Calibration
10. Bugs and Fixing
11. Final PoC System Demonstration 10/April 2023

Presentation Outline

- Problem Statement
- Target Objective
- Wish Specifications
- Isolation Techniques
- Market Survey Details
- System Level Block Diagram
- Core Component
- Preliminary Design

Problem statement:

High Voltage Differential Probe

- Tektronix P5200A
- Too high bandwidth & voltage range for UG lab use

100MHz, 1500V

Cons:

- Imported
- Only works with MDO Series Tek DSOs (or needs adapters)
- Too expensive **₹4,00,000**



Wish specifications:

- Voltage Range: **0-600V**
- Impedance: **10M Ω**
- Bandwidth: **DC-5Mhz**
- Common Mode Rejection Ratio (CMRR): **> 65dB**
- Signal Noise Ratio (SNR): **> 65dB**
- Isolation Voltage Rating: **1000V**
- Input Connector: **Banana jack type**
- Output Connector: **BNC**
- Operating Temperature: **10°C to 50°C**
- Power Source: **External**

Current Probe:

- Tektronix A622
- Too expensive ₹ 1,50,000
- Too high bandwidth for lab use
100kHz
- Imported

Target objective:

- Replacement of P5200A Device at low budget at 35k.



Isolation Techniques

- **RF, fibre optic, isolation mechanisms.**
- **RF Isolation** : It is used to protect your RF components from excessive power reflection.
- **RF Isolator** : An RF isolator is a 2-port device that transmits microwave or radio frequency power in one direction only while blocking the signal in the opposite direction.
- **RF ISOLATION TECHNIQUES:**
 - 1) **grounding techniques:**
 - It is used to have separate supplies for analog and digital sections of the chip to isolate the analog circuits from switching noise .

2)GUARD RINGS:

- current taken from a DC power source is properly isolated from the power source.
- The ring-guard isolation technique usually consists of three components: an insulating ring, a ground conductor, and a guard ring.

Pros:

Provide better isolation at lower frequencies

Cons:

At higher frequencies isolation becomes weak.

3)ON CHIP DECOUPLING:

- It improve signal integrity and reduce unwanted crosstalk between signals.
- The technique involves isolating the circuits or devices on the IC by using a dielectric material such as silicon dioxide (SiO₂) or polyimide (PI)..


Optical isolation

Principle:

Uses a LED or laser diode as light source, directed into a single mode optical fiber, which travels and then incident on photo detector (photodiode), this generates electrical signal.

Cons:

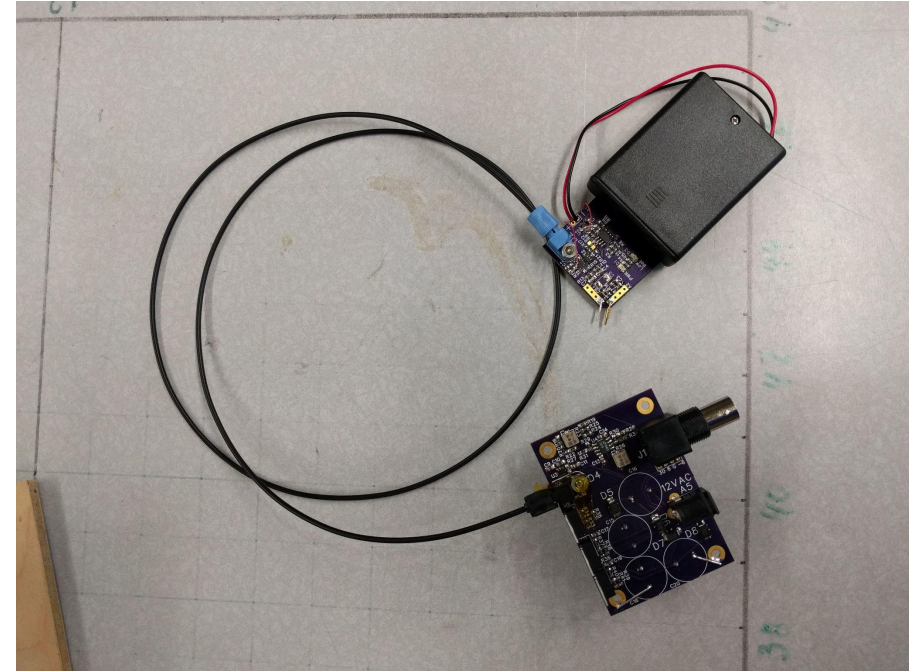
Low bandwidth, more delay, used in less input voltage, etc.



Fiber Optic isolated voltage probe

- 10x attenuation
- $\pm 50V$ input voltage range
- used battery for power supply
- it is noisy

Market Survey:

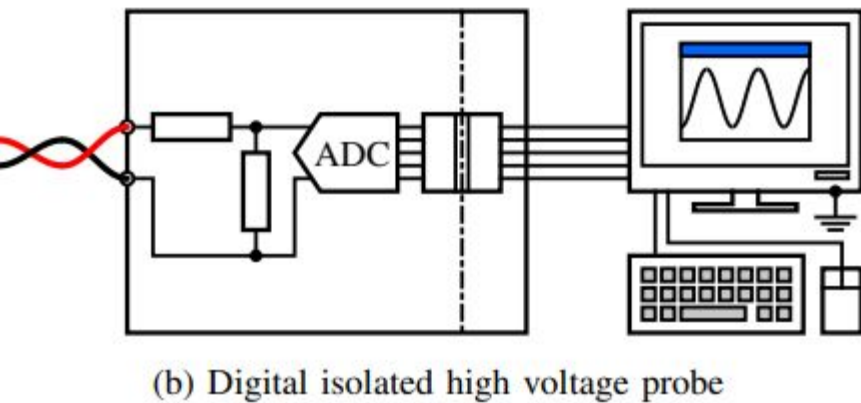

A Digital Isolated High Voltage Probe

In this probe isolation is provided by converting analog signals to digital using ADC and then isolating the digital data lines



High Voltage differential probe 25MHz , 400V input , same which we are targeting but not isolated.


Survey on isolated amplifiers



AMC1301QDWVQ1

Isolation Amplifiers Automotive
Precision +/-250mV-Input , Reinforced
Isolated Amplifier.

Price: ₹966.22

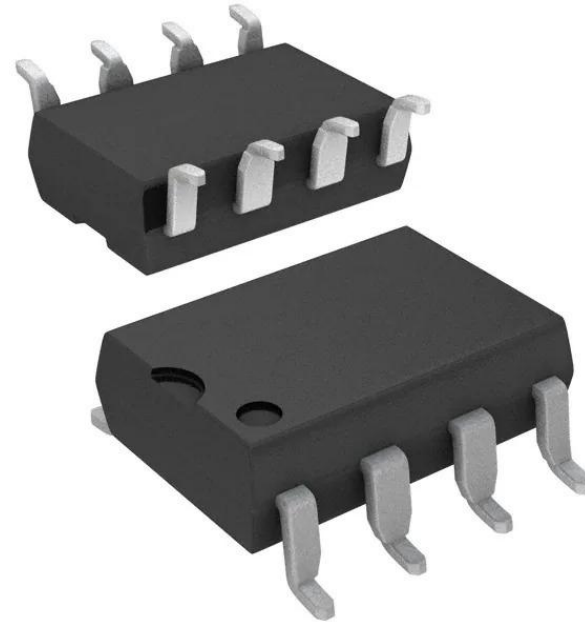

HCPL-7520-300E
optoisolator. Which
have ADC and DAC all
built in, and basically
only requires a power
supply on each side.
Although the
bandwidth is only
100kHz.

COST \$7

Core Component

(isolation amplifier)


AMC1301-Q1

- This barrier is certified to provide reinforced galvanic isolation of up to 7 kV peak.
- Specs
 - GBWP — 1000 kHz
 - CMRR — 92 dB
 - Operating Temperature — (-40 to 125 c)
 - VDD — (-0.3 to 7) V
 - Input Voltage Range — (GND1 – 6) to (VDD+ 0.5)



AMC1301-Q1


5 Pin Configuration and Functions

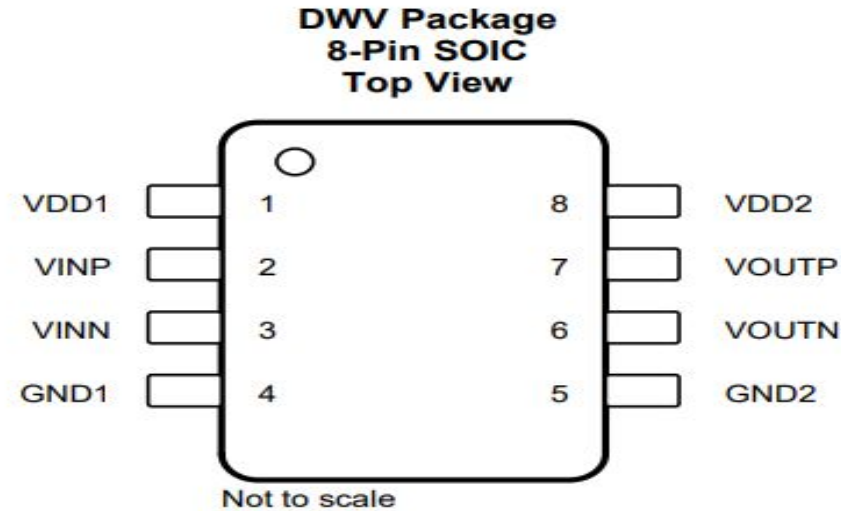

Pin Functions

PIN		I/O	DESCRIPTION
NAME	NO.		
GND1	4	—	High-side analog ground
GND2	5	—	Low-side analog ground
VDD1	1	—	High-side power supply, 3.0 V to 5.5 V. See the Power Supply Recommendations section for decoupling recommendations.
VDD2	8	—	Low-side power supply, 3.0 V to 5.5 V. See the Power Supply Recommendations section for decoupling recommendations.
VINN	3	I	Inverting analog input
VINP	2	I	Noninverting analog input
VOUTN	6	O	Inverting analog output
VOUTP	7	O	Noninverting analog output

● Rough Schematic of Circuit Diagram

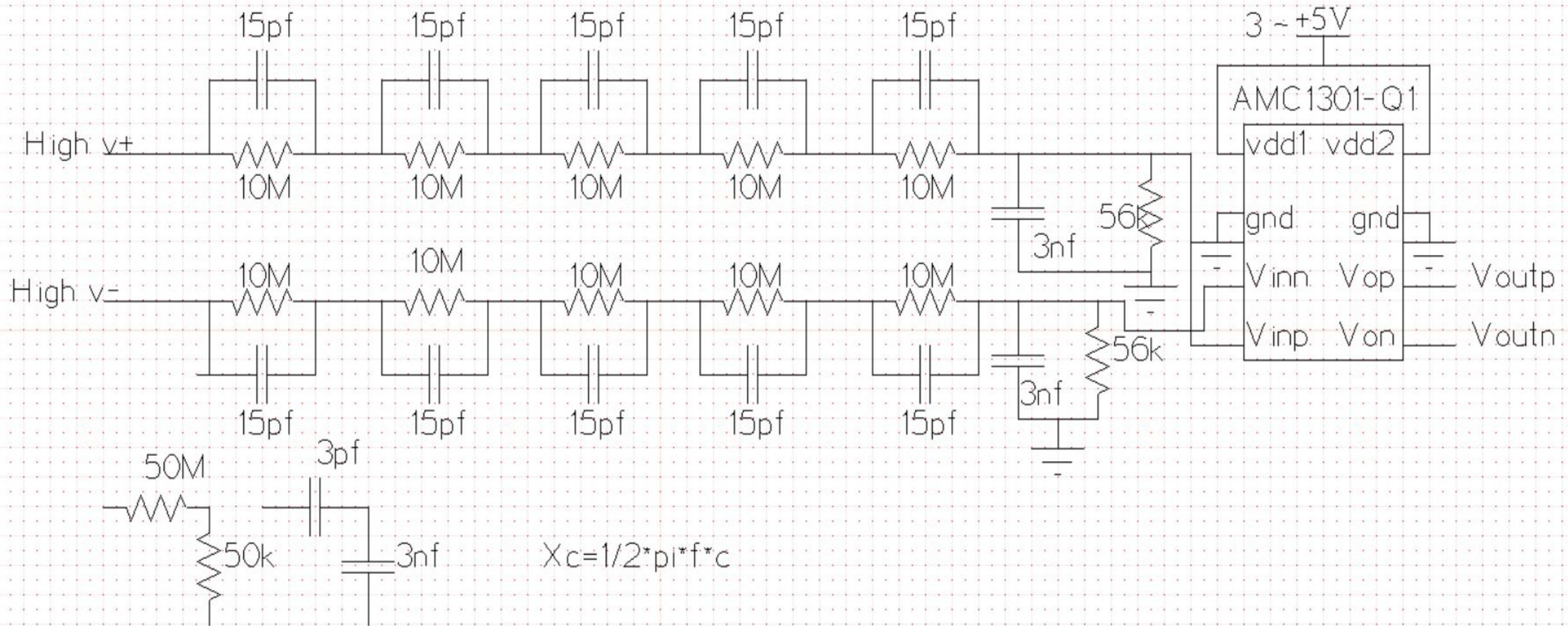


Future Work

Second Evaluation


1. Simulation
2. Prototyping
3. PCB design by 17/Feb 2023

THANK
YOU

System Block diagram

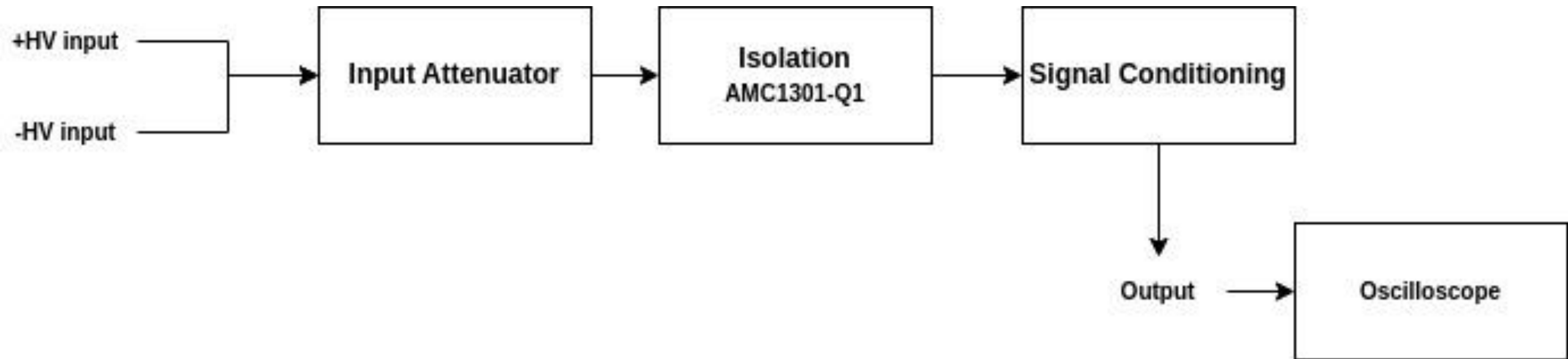


Input Attenuator Stage

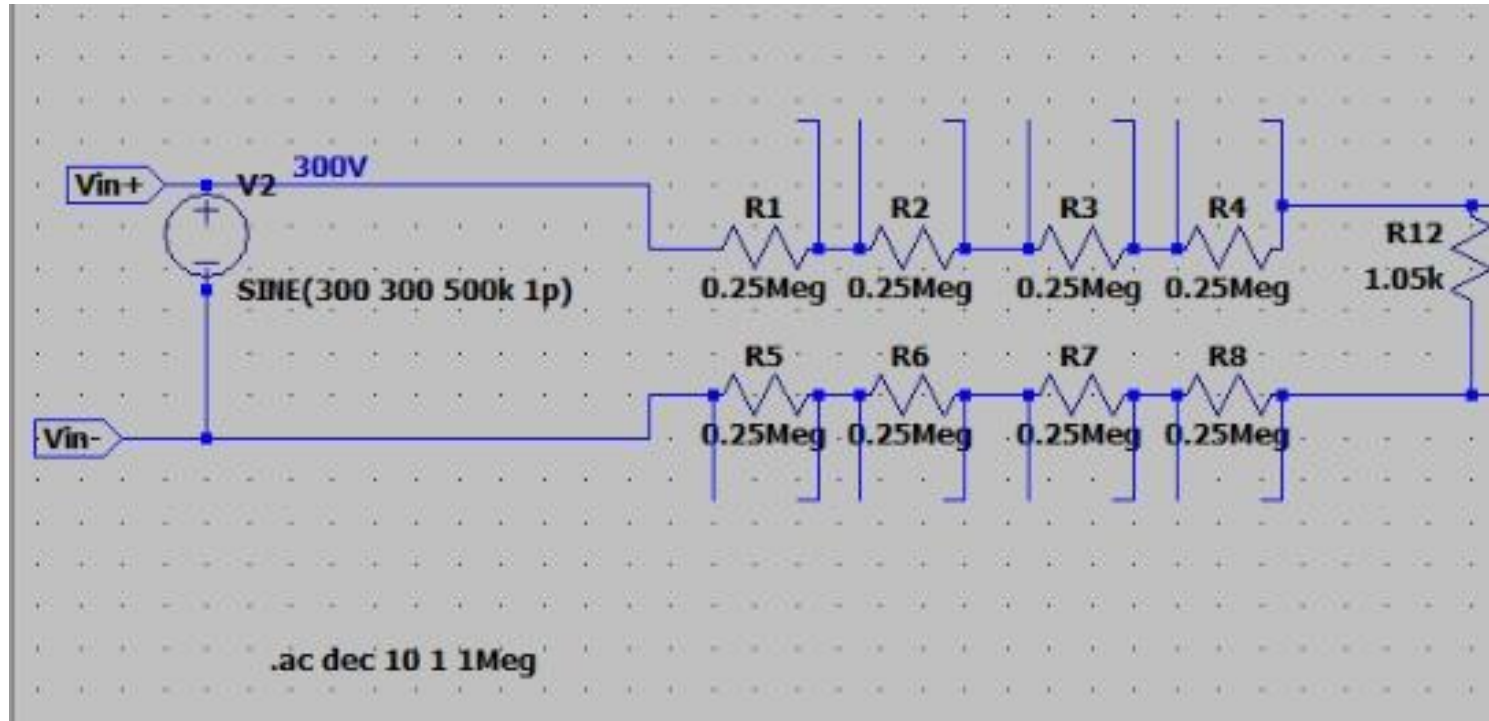

Attenuation: 1/2000

Isolated Amplifier Stage

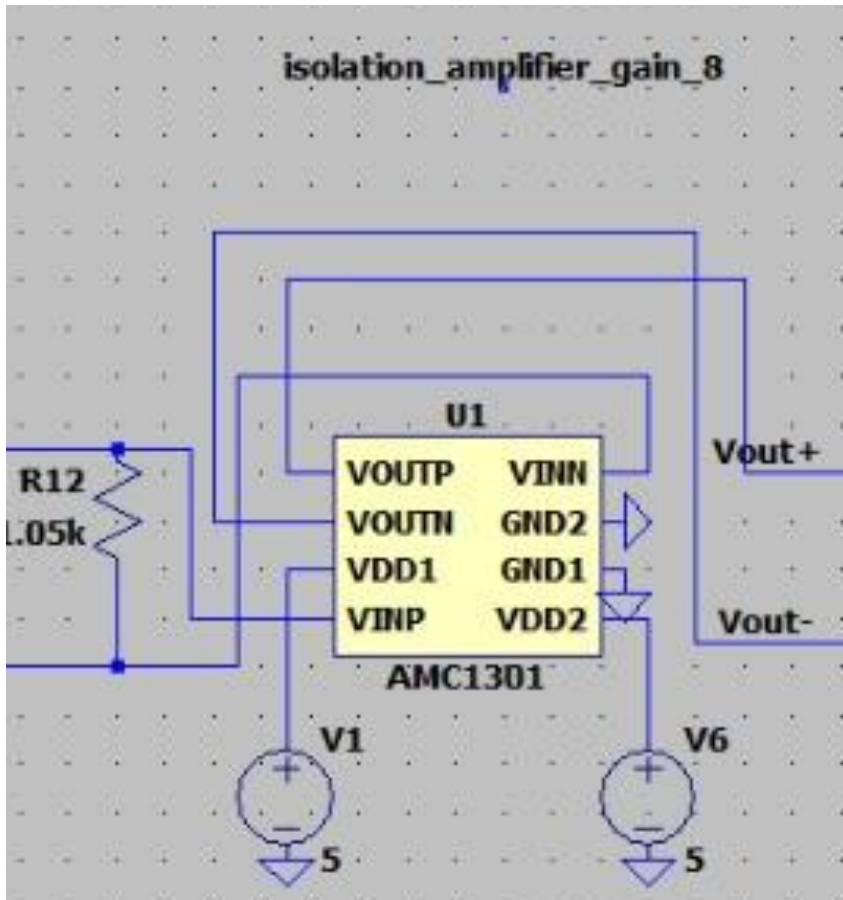

Bandwidth: 1MHz


gain: 8

Vdd: -0.3 to 7V

Input voltage range : 330mV (calculated by simulations)



Signal Conditioning

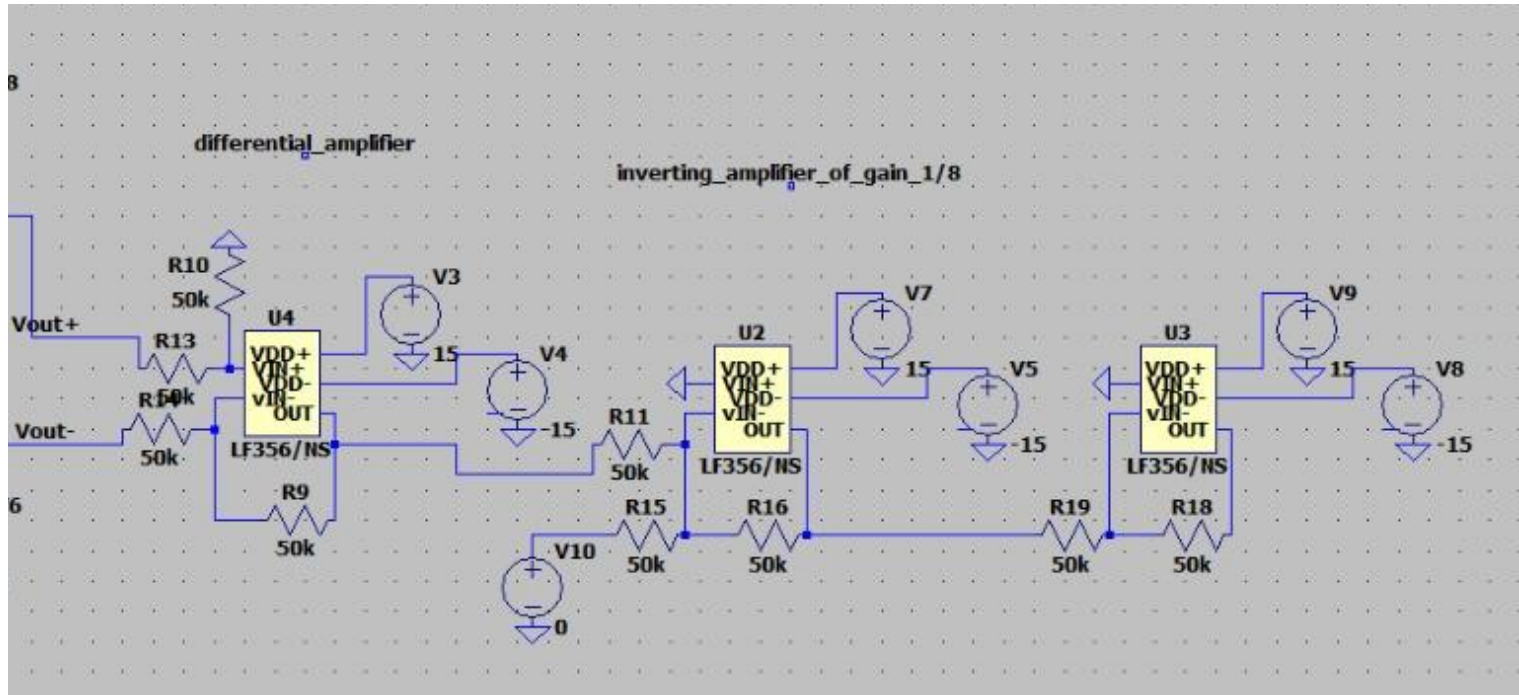

IC (LF356)


Differential amplifier : making output single ended

Inverting amplifier : used for trimming of gain and offset correction

Trimming Values Required for gain and offset correction

Frequency (Hz)	Gain (dB)	Trimming Values (Ohm)
1-10	-48.14	51075.(45892 to 45894)
10-100	-48.14	51075.(
100-1000	-48.14	
1000-10k	-48.14	
10k-100k	-48.15 - -48.71	
100k-1000k	-48.71 - -114.8	

Circuit Schematic

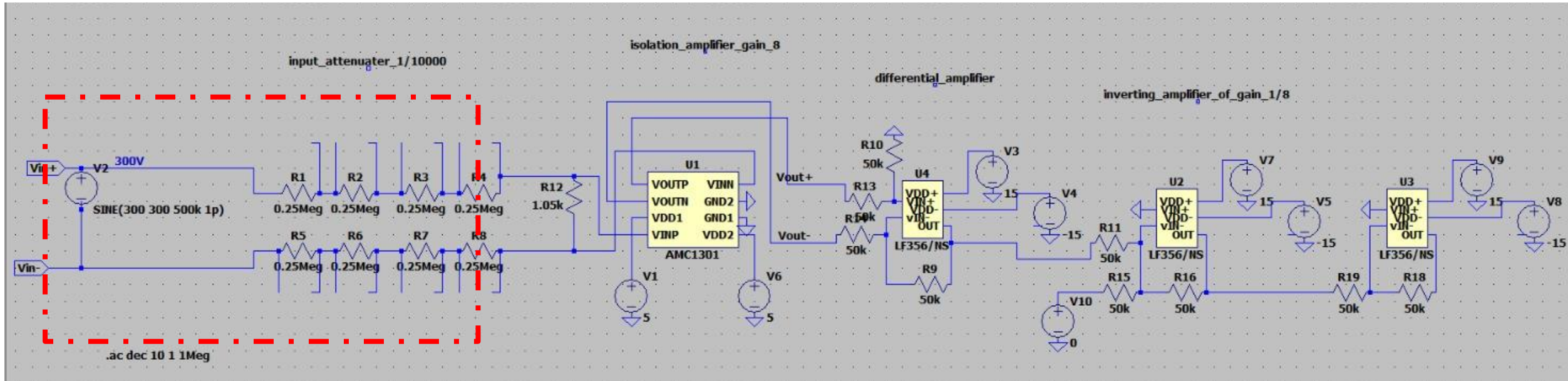

Stages:

Input attenuator(voltage divider)


isolation amplifier (AMC1301 IC) (bandwidth=1000kHz)

differential amplifier


inverting amplifier (for gain correction)

inverting amplifier (for offset correction)

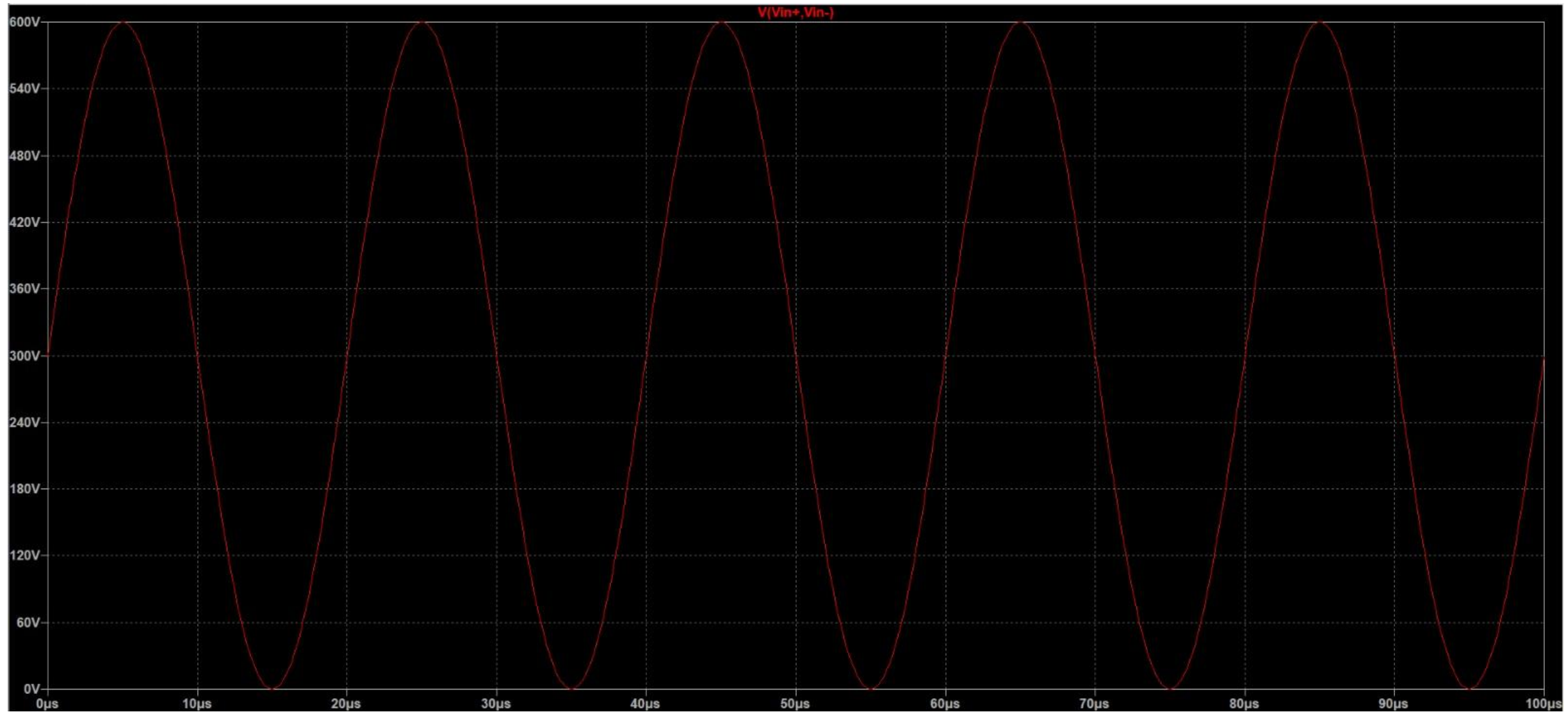
High Voltage Input plot ($\pm 600\text{V}$)



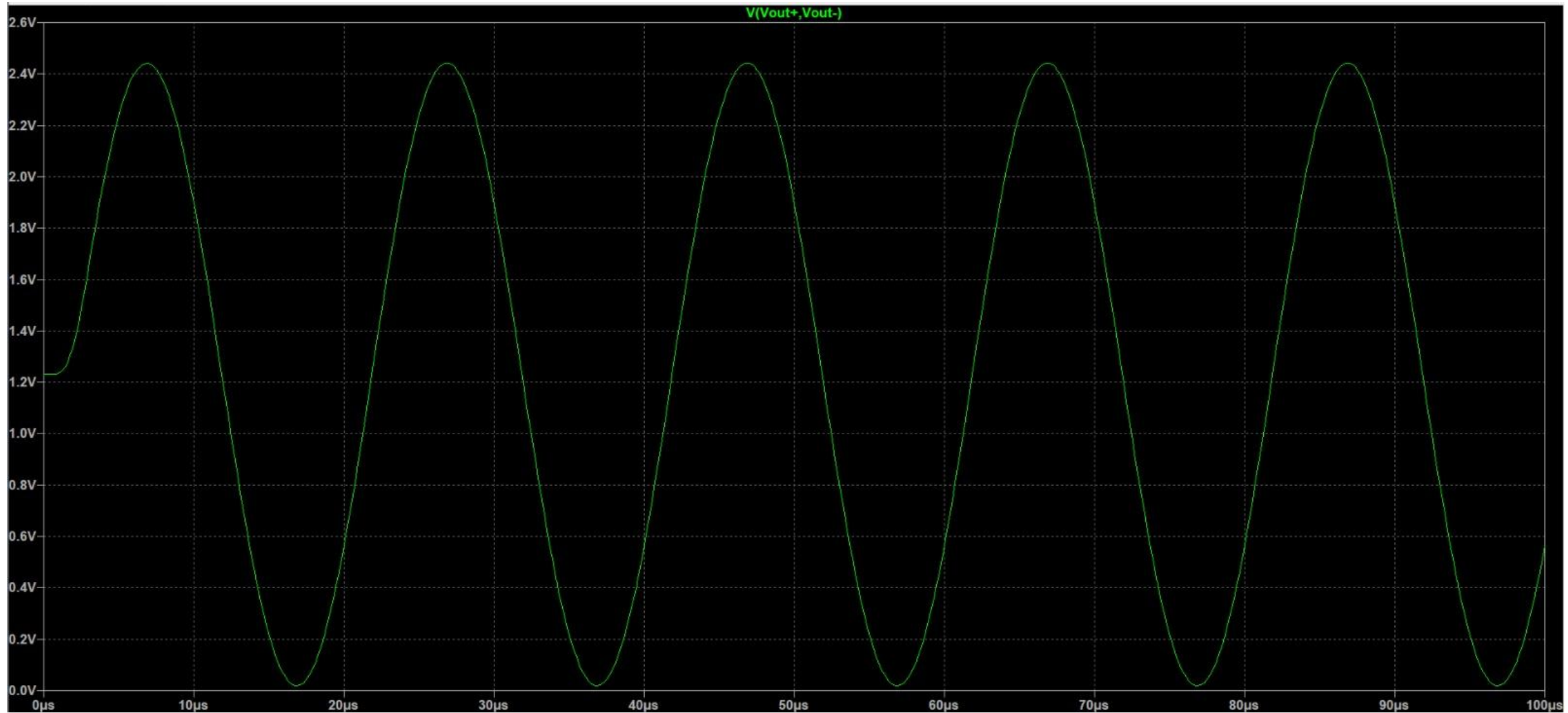
AC analysis Output after Isolated amplifier stage



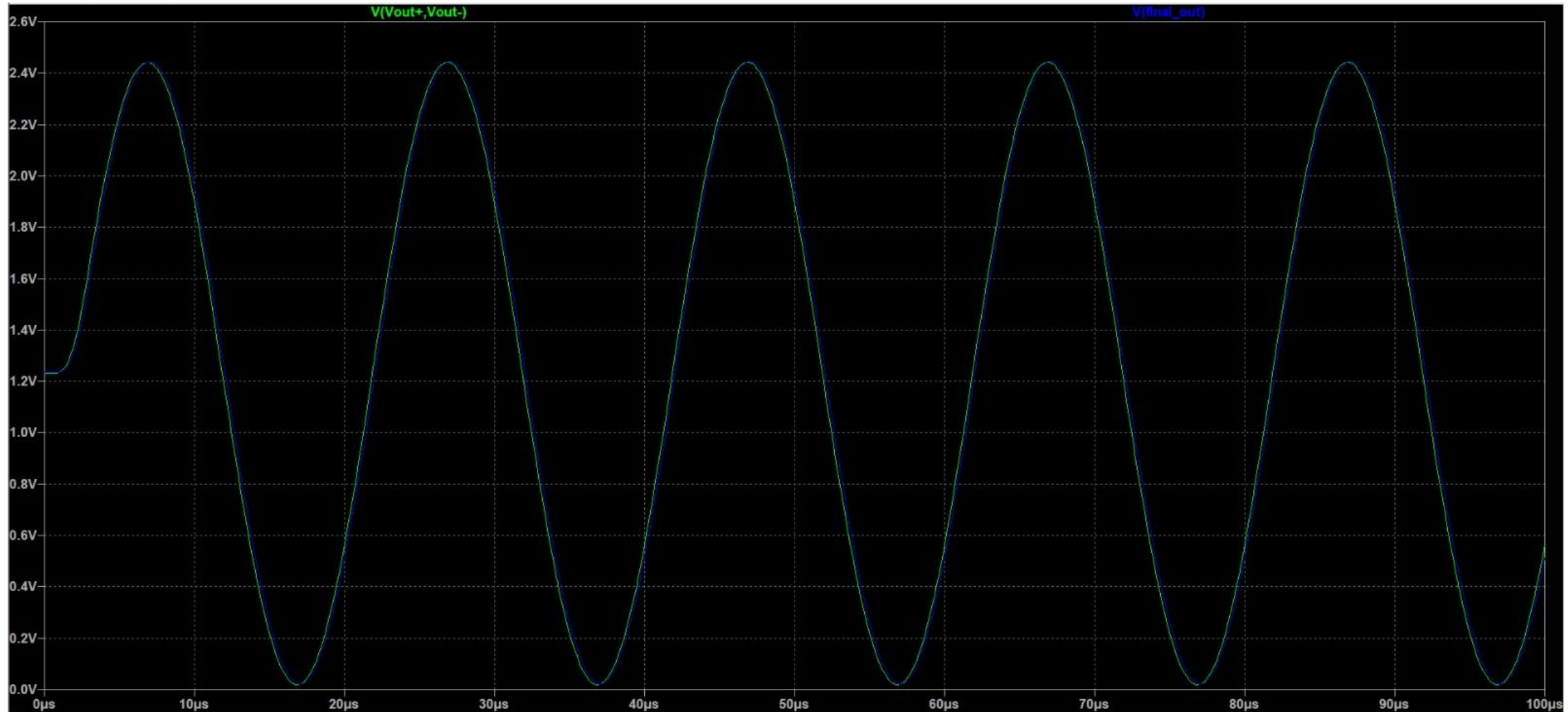
Output after differential amplifier vs output after Isolated amplifier



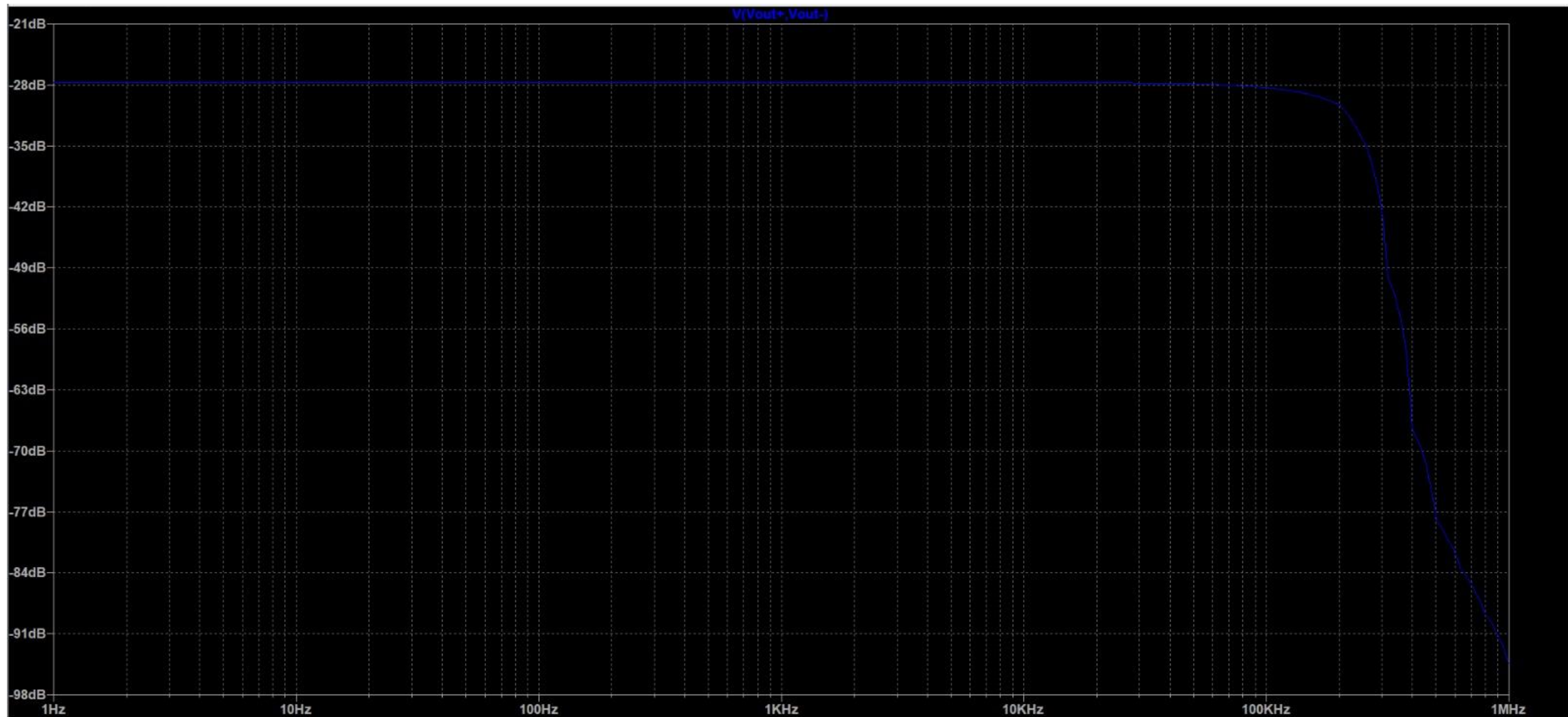
Transient analysis Output after Isolated amplifier stage



PCB schematic diagram

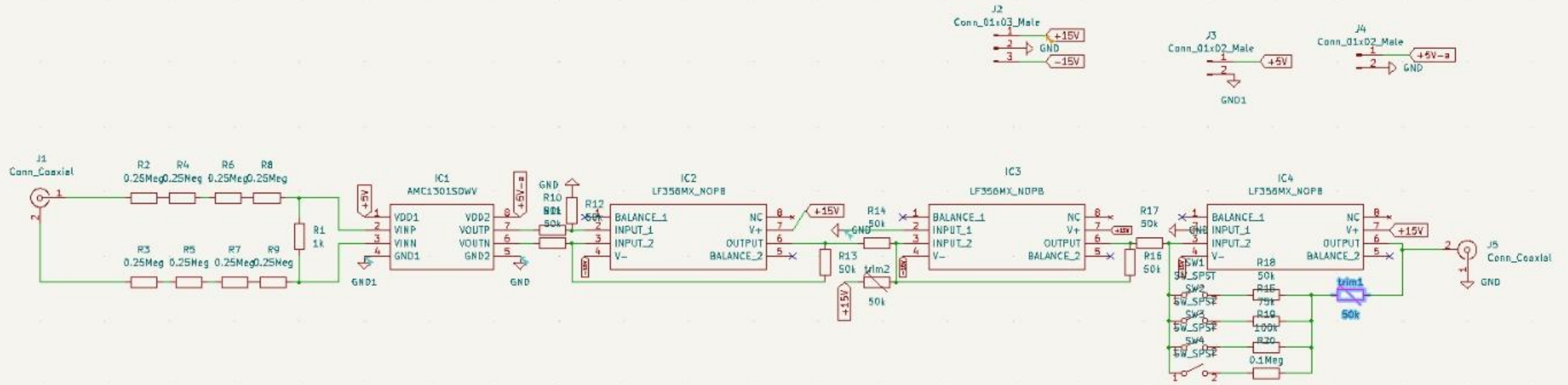

PCB Design

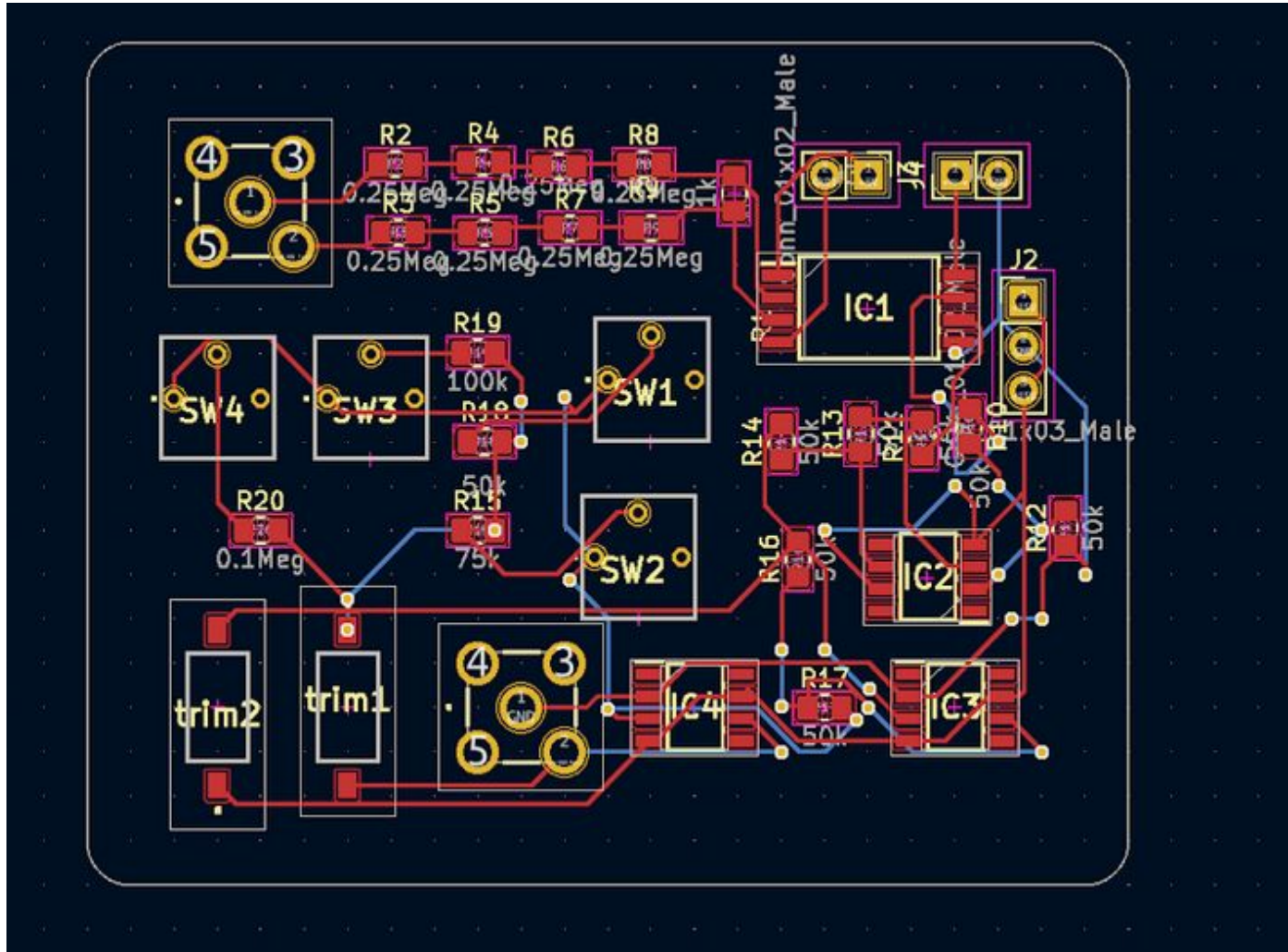

3D model of PCB Design

