



॥ सा विद्या या विमुक्तये ॥


भारतीय प्रौद्योगिकी संस्थान धारवाड़

Indian Institute of Technology Dharwad


High Voltage Isolated Differential Probe

Wish specifications:

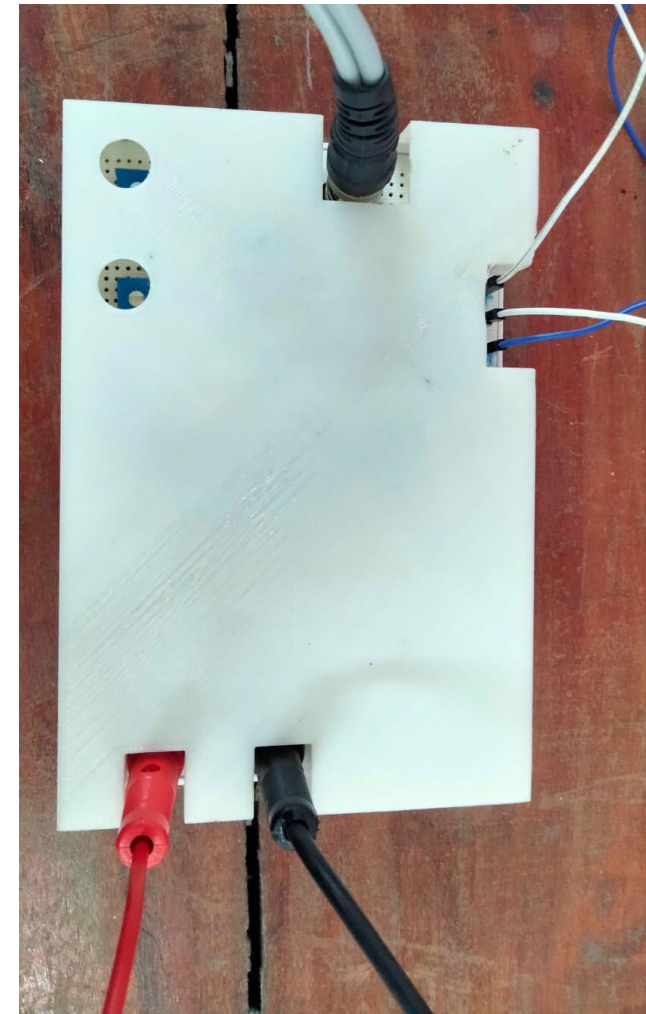
- Voltage Range: **0-600V**
- Bandwidth: **DC-125KHz**
- Isolation Voltage Rating: **1000V**
- Input Connector: **Banana jack type**
- Output Connector: **BNC**
- Operating Temperature: **10°C to 50°C**
- Power Source: **External,Batteries**



System Block diagram

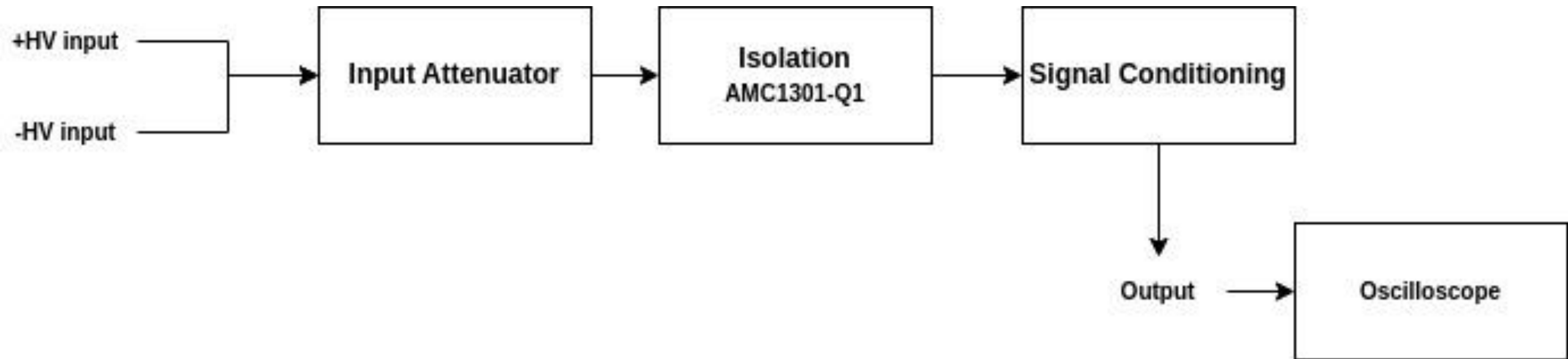


Input Attenuator Stage

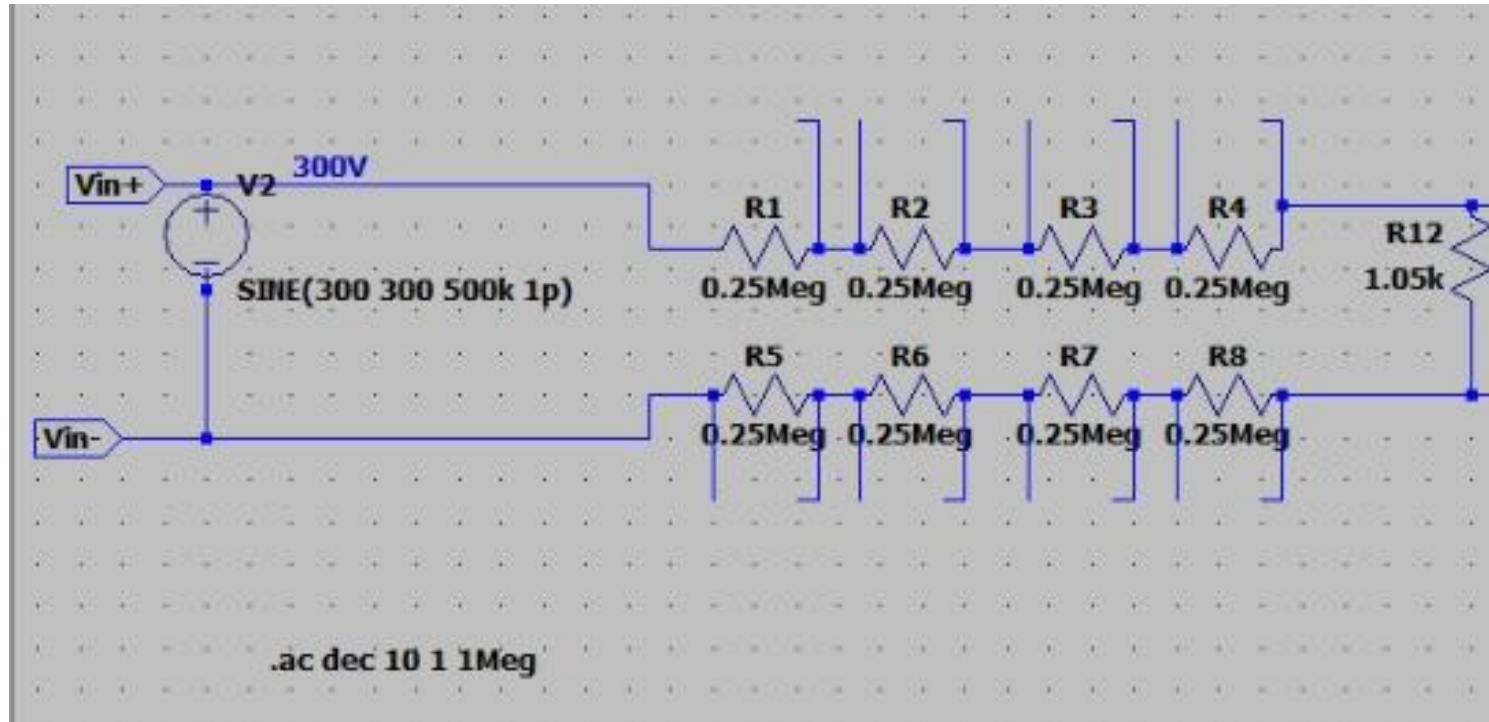

Attenuation: 1/2000

Isolated Amplifier Stage

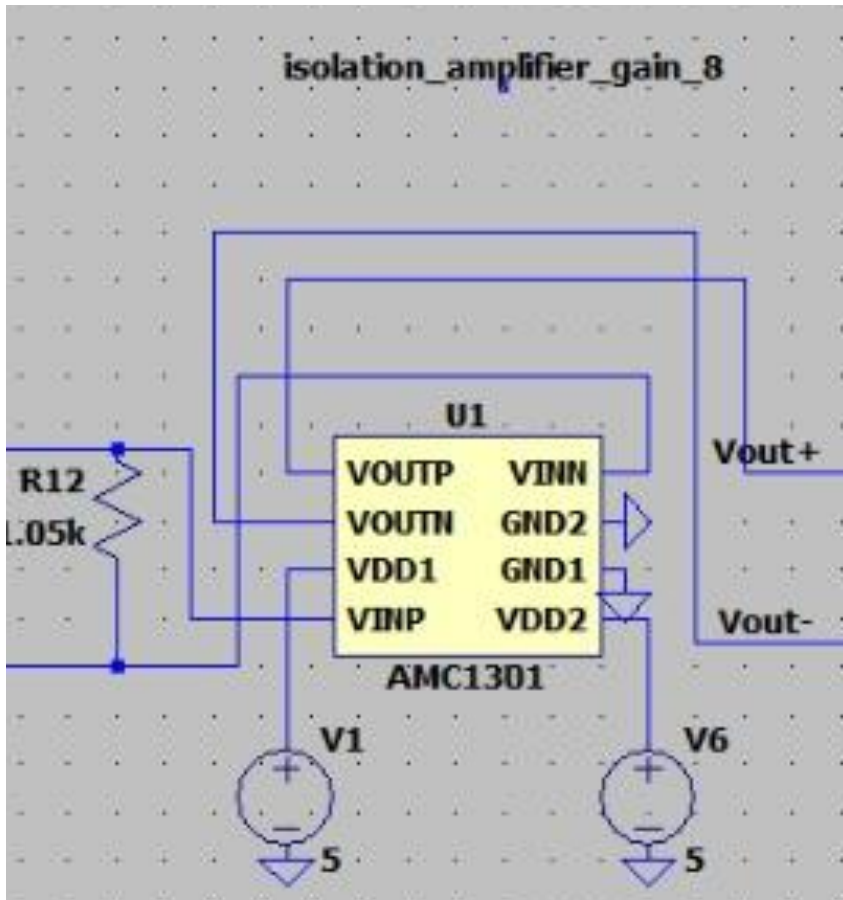


Bandwidth: 1MHz

gain: 8

Vdd: -0.3 to 7V

Input voltage range : 330mV (calculated by simulations)

Signal Conditioning


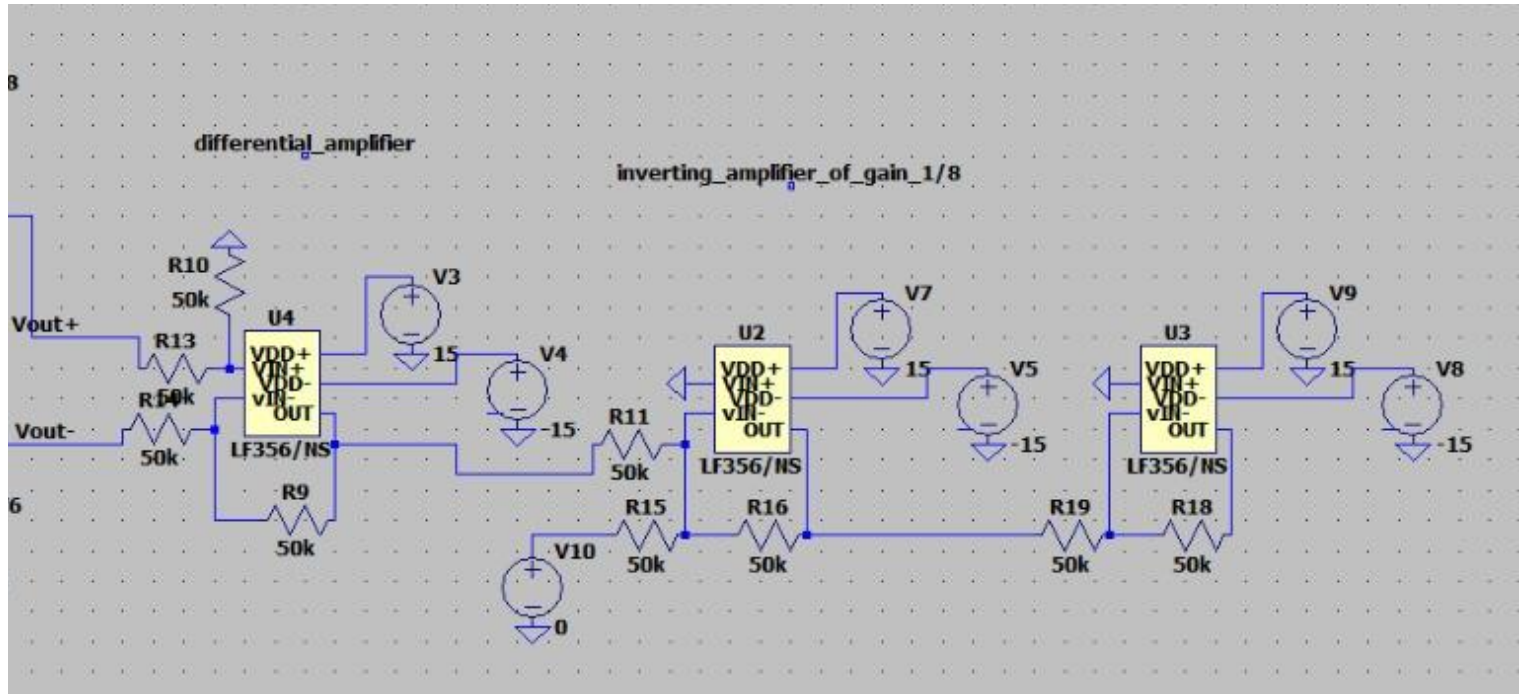


IC (LF356)

Differential amplifier : making output single ended



Inverting amplifier : used for trimming of gain and offset correction

Circuit diagram

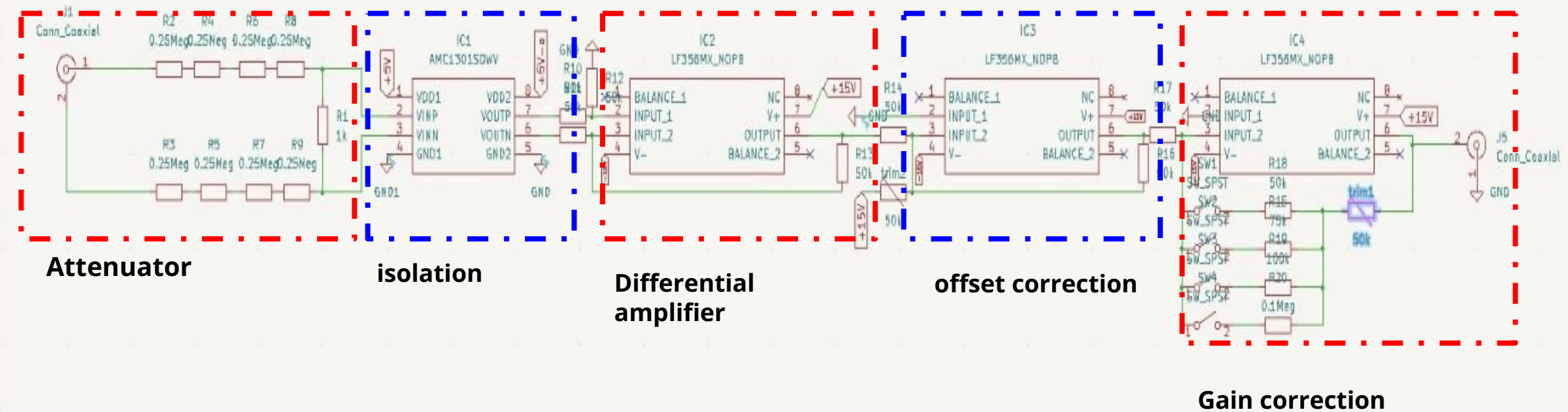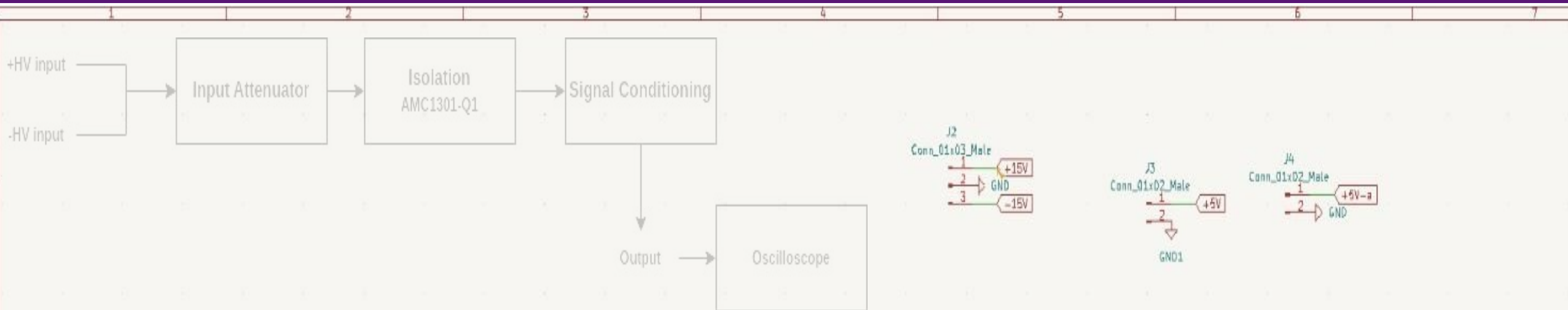

At an input of 200rms

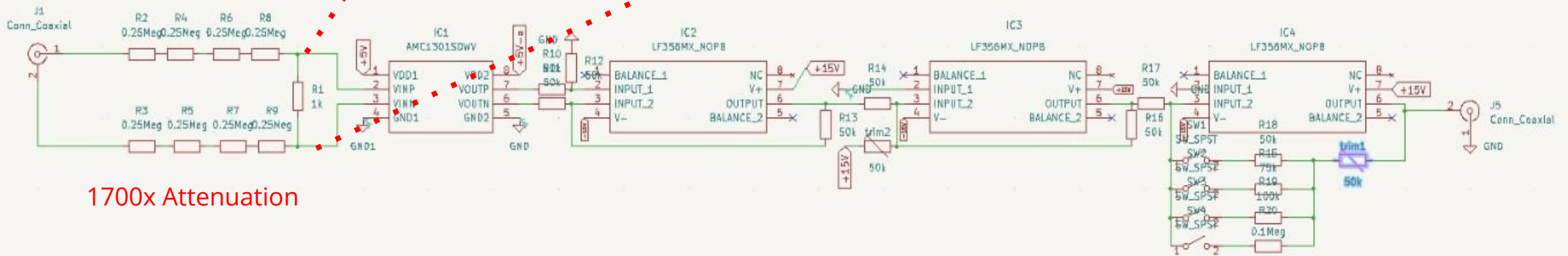
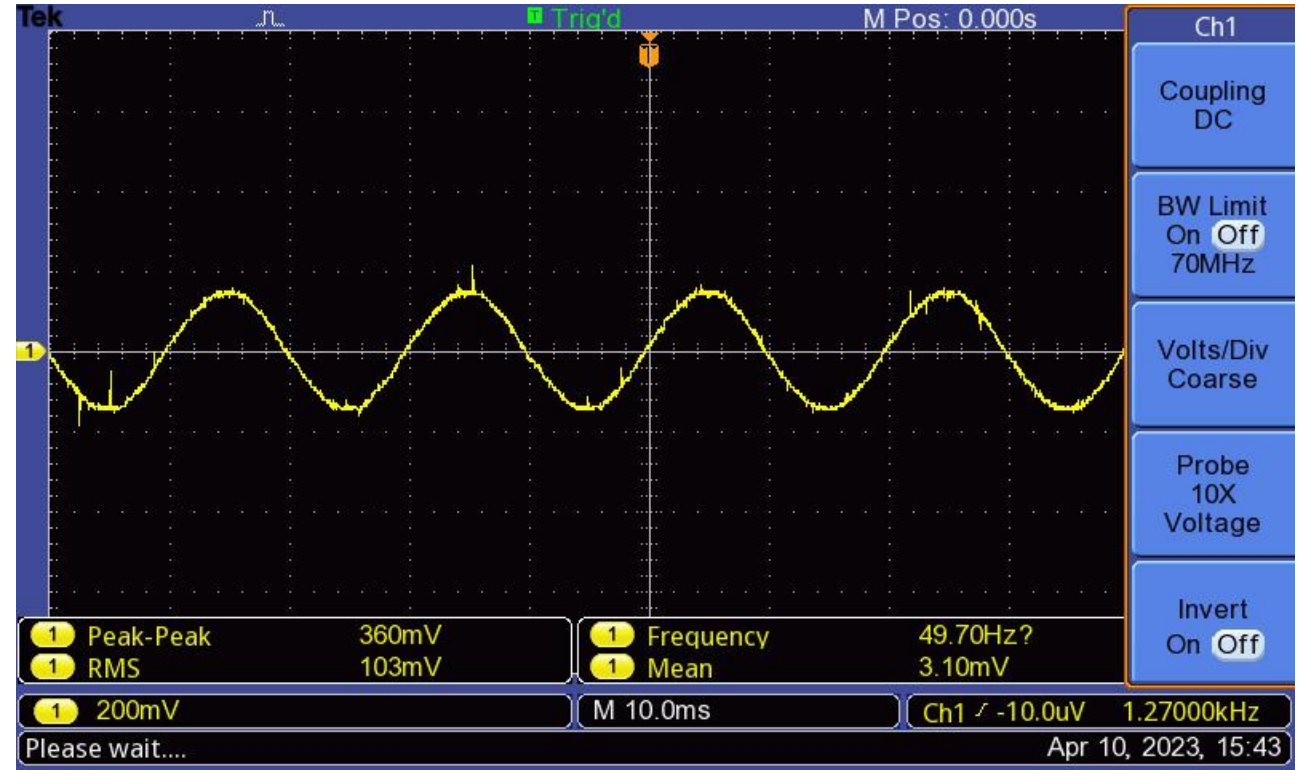
Expected = $200V / 1888 = 105mV$
Obtained = 103mV



1700x Attenuation



At an input of 200 mv pp to isolation amplifier at 2 kHz

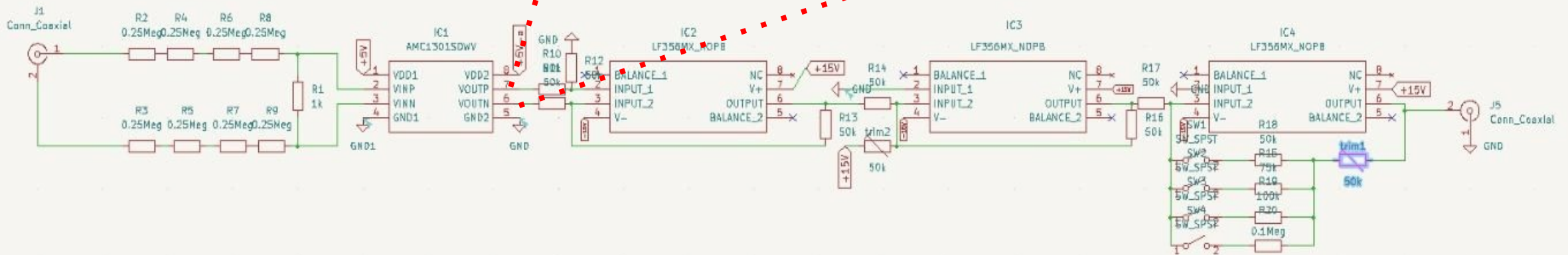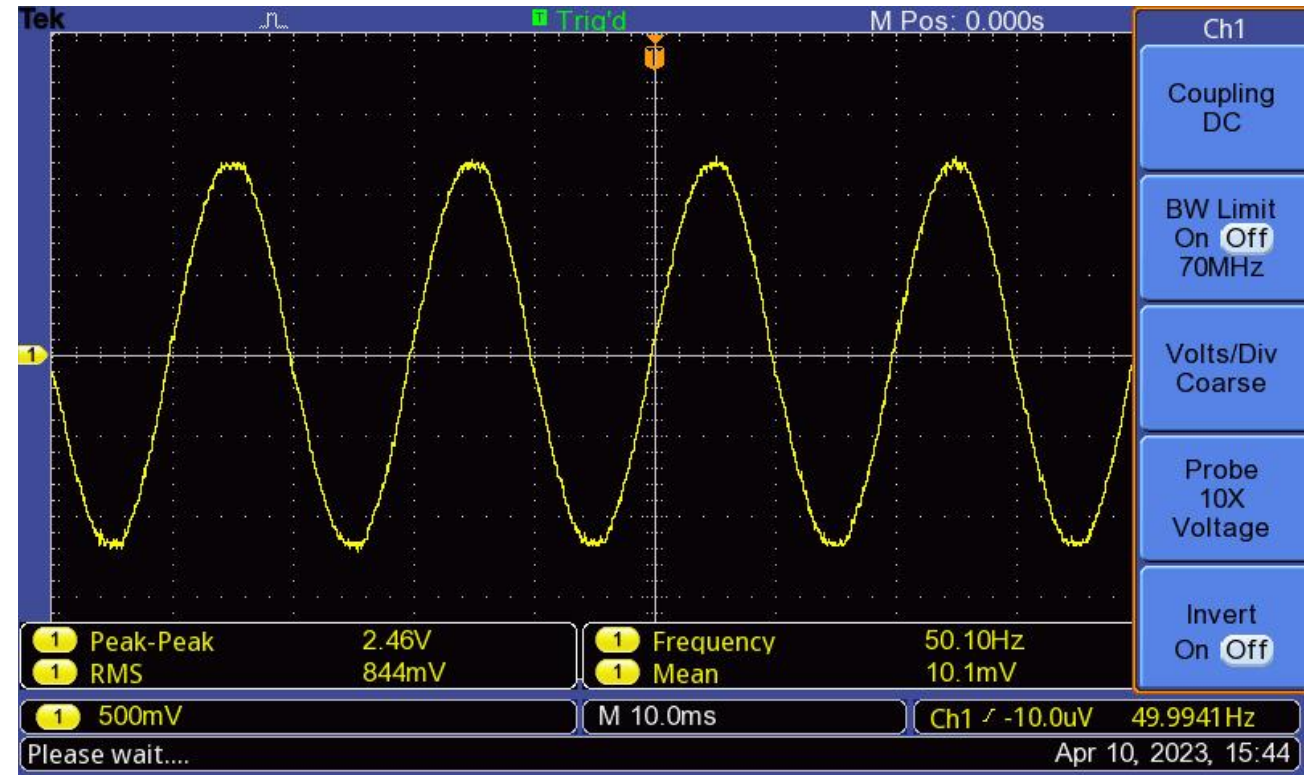Expected gain = 8
expected output = 824mV
obtained output = 844mV



Differential Amplifier

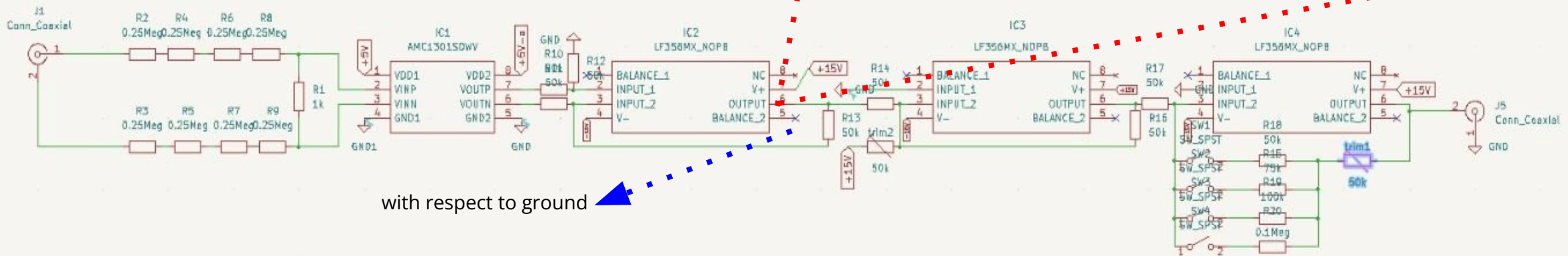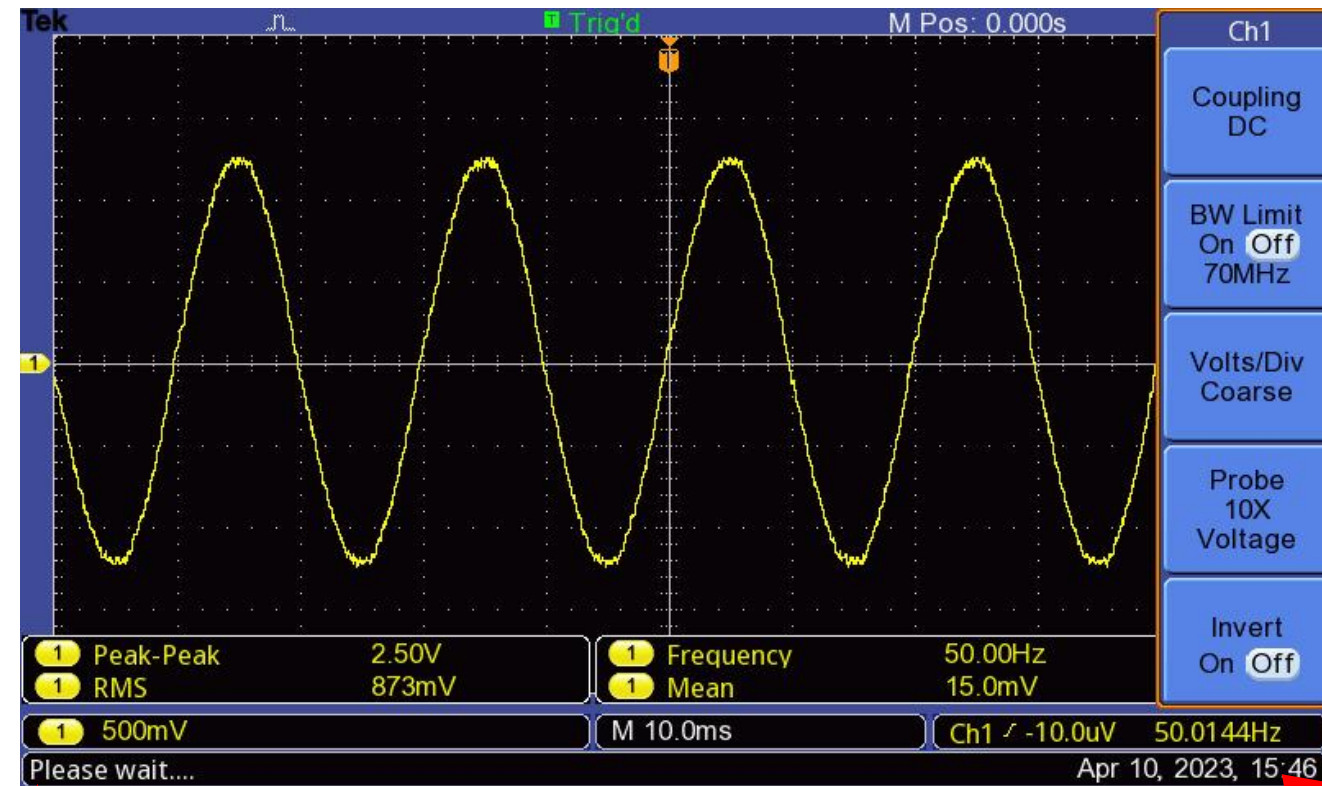Gain = 1
 expected output = 844mV
 obtained output = 873mV





Summing amplifier(offset correction)

Gain = 1

expected output = 873mV

obtained output = 880 mV

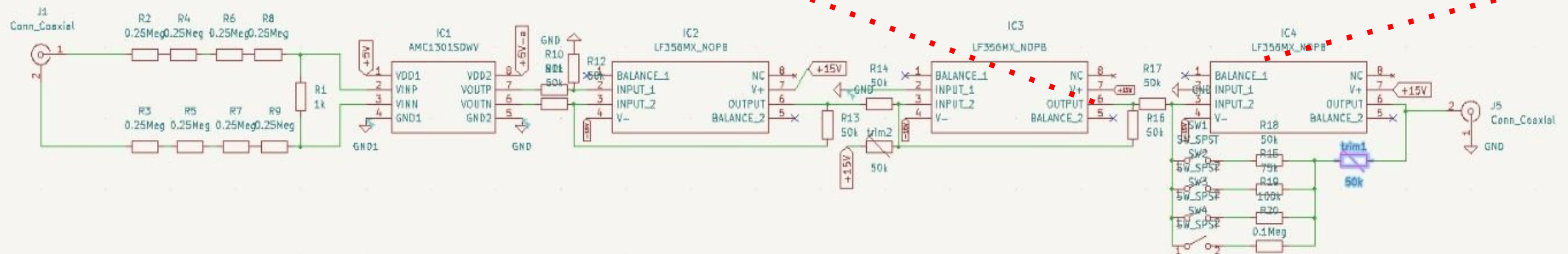
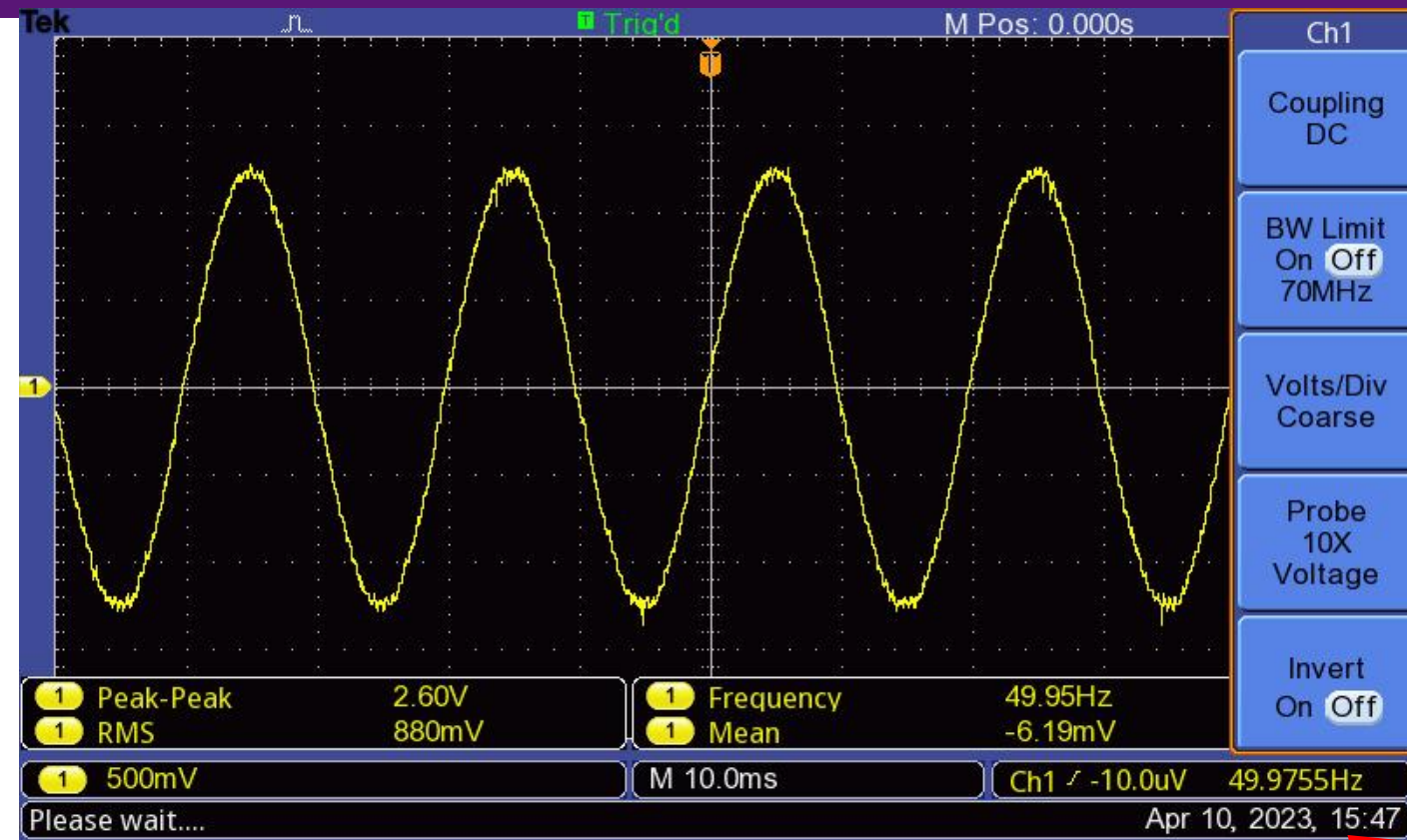
NEGATIVE AND POSITIVE OFFSET
CORRECTION CAN BE DONE.




Inverting amplifier (Gain Correction)


Gain = adjustable.
expected output = 880mV
obtained output = 875mV

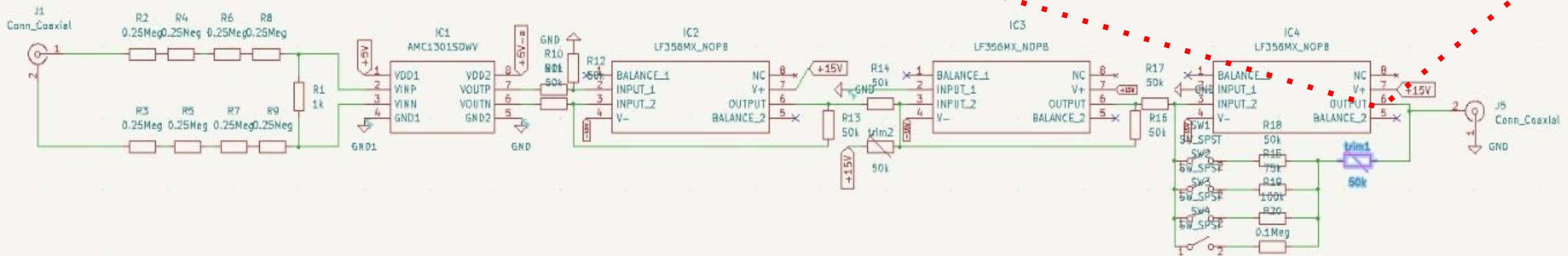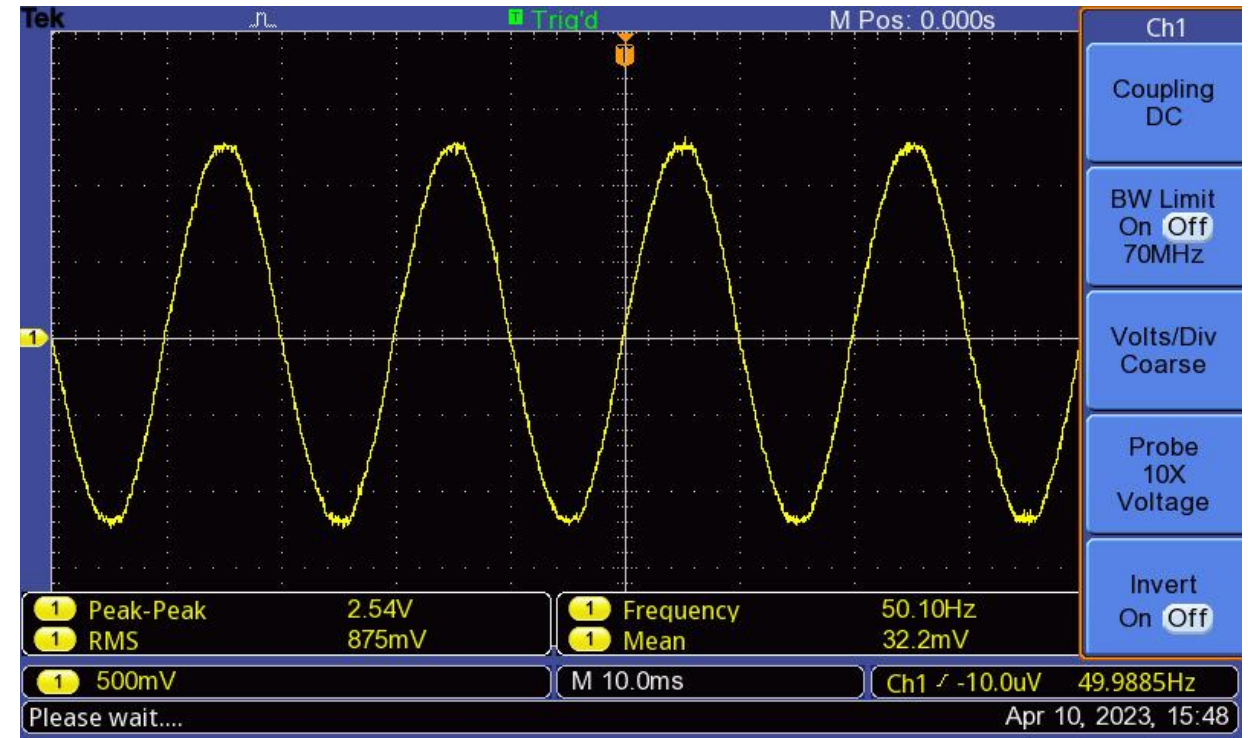NEGATIVE AND POSITIVE GAIN
CORRECTION CAN BE DONE.



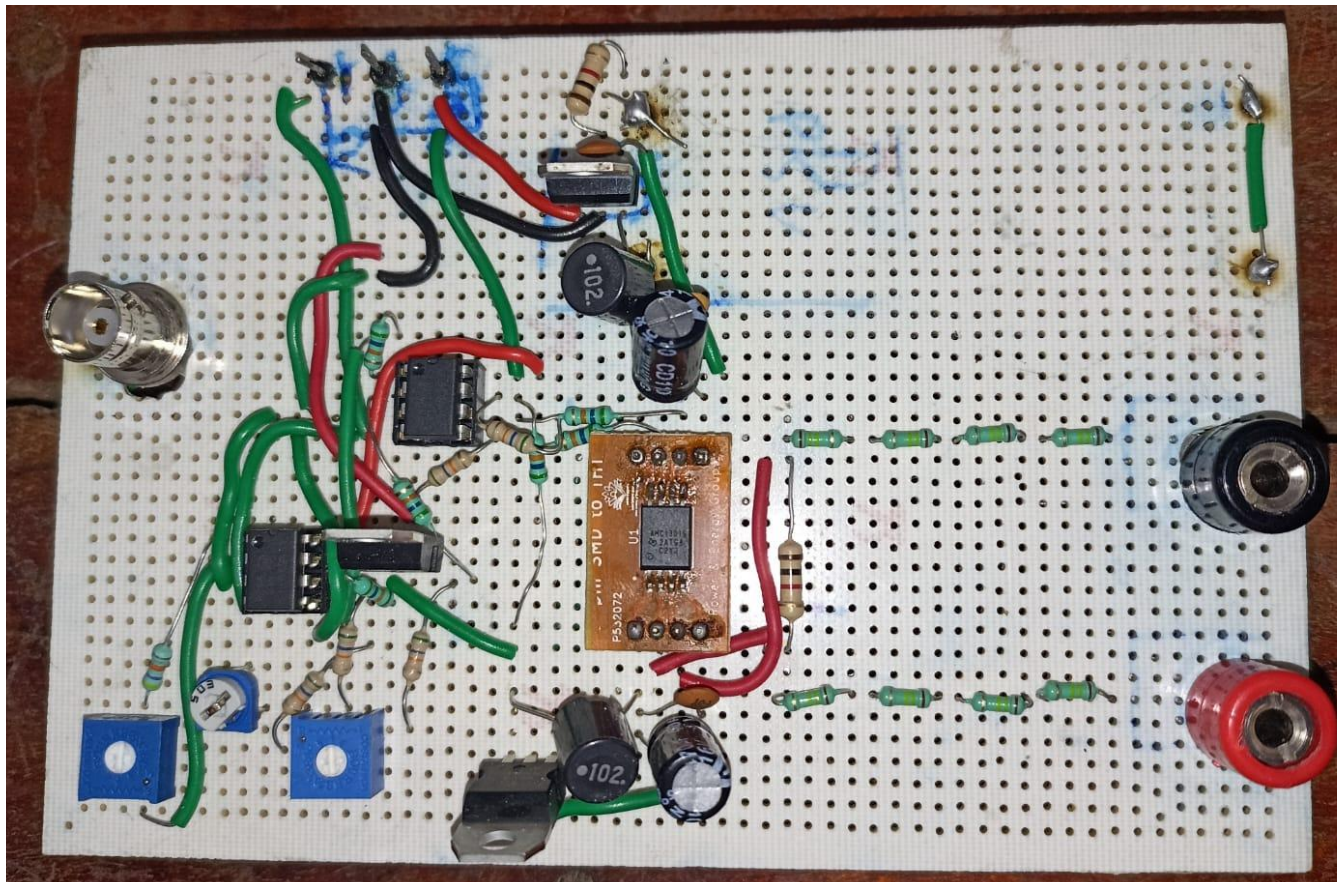

Front Side

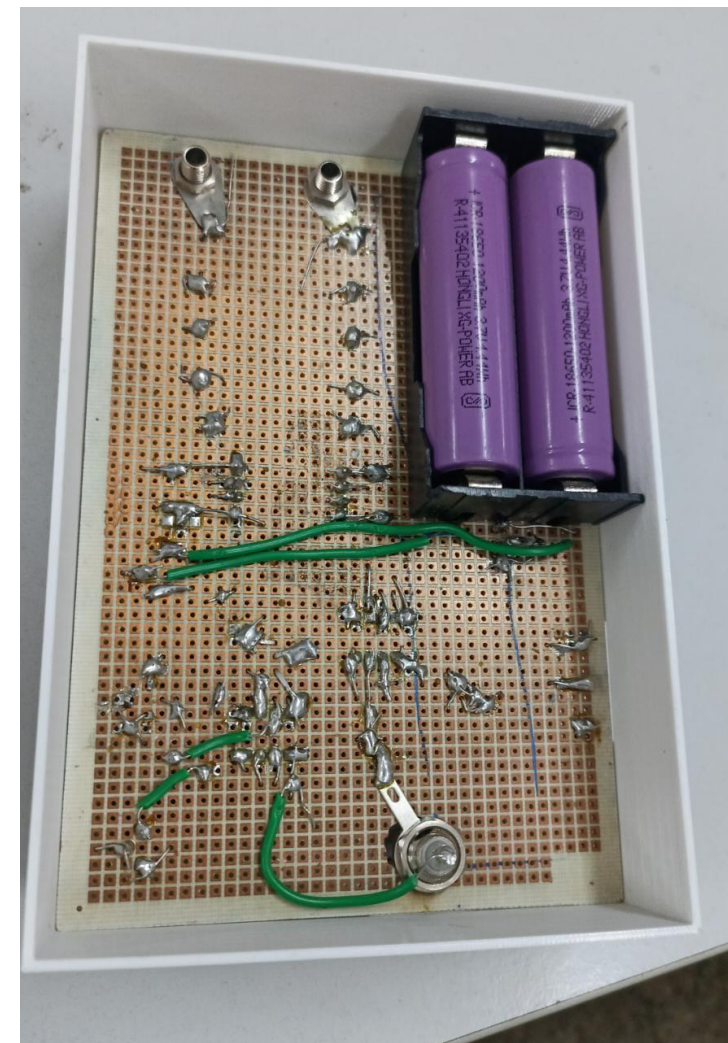

Back Side

THANK YOU